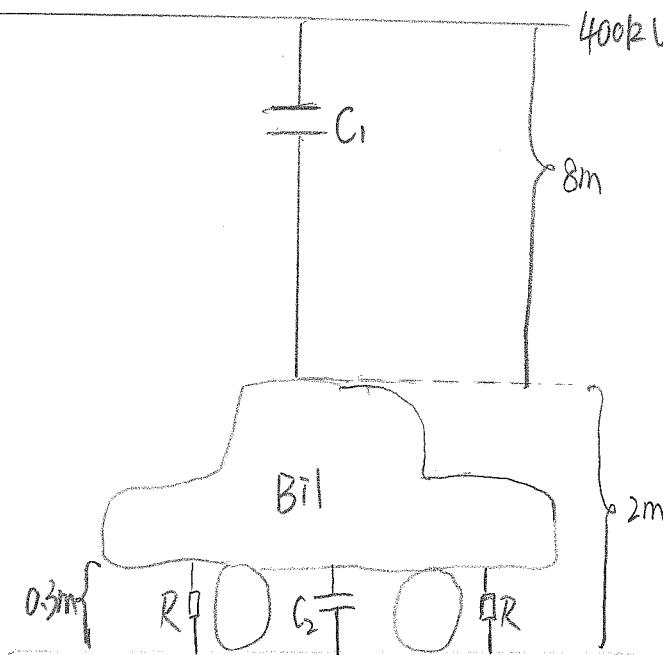


2008-01-17


Problem #1

①

a)



b)

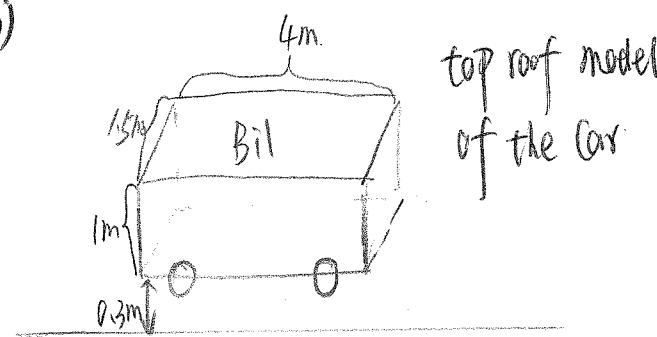

$$A_{\text{eff}} = A_{\text{top}} + \text{"edge effect"}$$


$$\approx 10 \text{ m}^2$$

$$d_1 = 8 \text{ m}$$

$$d_2 = 0.3 \text{ m}$$

$$C = \frac{\epsilon A}{d} \Rightarrow C_1 = \frac{\epsilon_0 \cdot 10}{8} F \approx 11 \text{ PF}$$
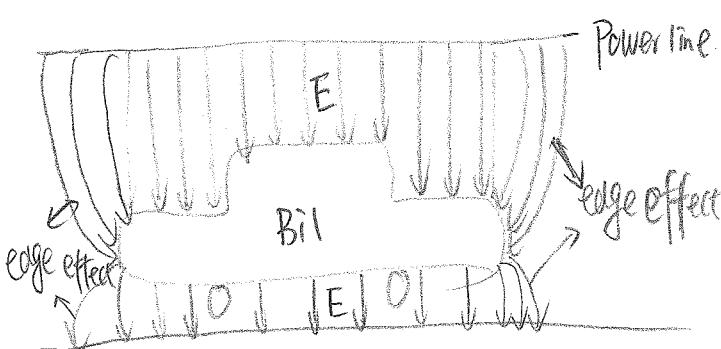
$$C_2 = \frac{\epsilon_0 \cdot 10}{0.3} F \approx 0.3 \text{ nF}$$




$R = 0$. good isolator.

2008-01-17

(3)

Problem #2

a)

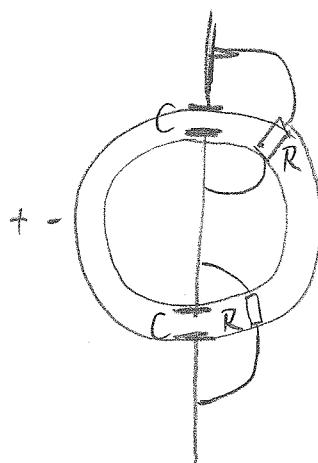b) Cell diameter $D = 50 \mu\text{m}$, membrane thickness $d = 10 \text{ nm}$. Voltage across membrane: $V = 70 \text{ mV}$

$$C_{\text{membrane}} = \frac{CA}{d} = \frac{10^6 \epsilon_0 \cdot \left(\frac{50 \cdot 10^{-6}}{2}\right)^2 \pi}{10 \cdot 10^{-9}} \approx 1.74 \mu\text{F}$$

$$R_{\text{membrane}} = \frac{d}{\sigma A} = \frac{10 \cdot 10^{-9}}{0.1 \left(\frac{50 \cdot 10^{-6}}{2}\right)^2 \pi} \approx 50.9 \text{ n}\Omega$$

$$C) Z_{\text{total}} = \frac{1}{1/R_{\text{membrane}} + j\omega C_{\text{membrane}}} \approx 50.86 - j1.415(\text{n})$$


$$|I| = \frac{|V|}{|Z|} = \frac{70 \cdot 10^{-3}}{|Z_{\text{total}}|} = \frac{70 \cdot 10^{-3}}{\sqrt{50.86^2 + 1.415^2}} \approx 1.3758 \cdot 10^{-3} \text{ A} \approx 1.3758 \text{ mA}$$

① the liquid is not perfect conductor, and due to the finite conductivity, there must be some loss there.

② the model we used is based on rectangular geometry, while the cell is not rectangular shaped

C)

(2)

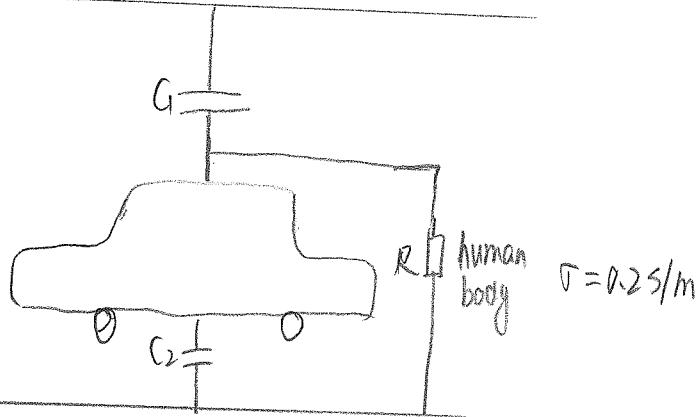

Suppose $f = 50\text{Hz}$.

$$R = \frac{l}{A\tau} \approx \frac{1.7}{0.3 \cdot 0.3 \cdot 0.2} = 100\Omega.$$

$$\begin{aligned} Z_{\text{total}} &= \frac{1}{j\omega C_1} + \frac{1}{j\omega C_2} + \frac{1}{R_{\text{body}}} = -j2.88 \cdot 10^8 + \frac{1}{j9.27 \cdot 10^{-8} + 0.01} \\ &\approx -j2.88 \cdot 10^8 + \frac{1}{0.01} \quad \rightarrow \text{very small} \\ &\approx -j2.88 \cdot 10^8 \quad \rightarrow \text{Very small also} \end{aligned}$$

$$I_{\text{body}} = \frac{V}{Z_{\text{total}}} = \frac{V}{\frac{1}{j\omega C_1}} = j\omega C_1 V = j\omega C_1 A E.$$

$$E = \frac{V}{d} = \frac{400\text{kV}}{8\text{m}} = 50\text{kV/m}$$

$$A = 10\text{m}^2$$

$$|I_{\text{body}}| = \omega C_1 A E = 2\pi \cdot 50 \cdot 8.86 \cdot 10^{-12} \cdot 50 \times 10^3 \approx 1.4\text{mA}$$

d) NO danger. It becomes dangerous when it is more than 5mA

2008-01-17 (2007-06-02 Problem #3)

④

Problem #3

$$U_2 = \frac{R_1}{R_1 + \frac{1}{\omega C}} \quad \text{a1}$$

$$\Rightarrow \frac{U_2}{U_1} = \frac{R_1}{R_1 + \frac{1}{\omega C}} = \frac{R_1}{R_1 - \frac{1}{\omega C}} = \frac{R_1(R_1 + \frac{1}{\omega C})}{(R_1^2 + \frac{1}{\omega C^2})} = \frac{R_1^2 + j\frac{R_1}{\omega C}}{R_1^2 + \frac{1}{\omega C^2}}$$

$$\Rightarrow \frac{U_2}{U_1} = \frac{W^2 R_1^2 + j\omega C R_1}{1 + W^2 C^2 R_1^2}$$

$$\Rightarrow |H(\omega)| = \sqrt{\frac{W^2 C^2 R_1^2}{(1 + W^2 C^2 R_1^2)^2} + \frac{W^4 C^4 R_1^4}{(1 + W^2 C^2 R_1^2)^2}}$$

$$= \frac{W C R_1 \sqrt{1 + W^2 C^2 R_1^2}}{1 + W^2 C^2 R_1^2}$$

$$\frac{W C R_1 \sqrt{1 + W^2 C^2 R_1^2}}{1 + W^2 C^2 R_1^2} = \frac{1}{f_2} \Rightarrow \frac{W^2 C^2 R_1^2 (1 + W^2 C^2 R_1^2)}{(1 + W^2 C^2 R_1^2)^2} = \frac{1}{2}$$

$$\Rightarrow \frac{1 + W^2 C^2 R_1^2}{2} = W^2 C^2 R_1^2 \quad f_u = \frac{1}{2\pi \cdot 47 \cdot 10^9 R_1} = 100$$

$$\Rightarrow W^2 C^2 R_1^2 = 1 \quad \Rightarrow R_1 = \frac{1}{2\pi \cdot 47 \cdot 10^9 \cdot 100} \\ = 33 \cdot 10^5 \Omega$$

$$\Rightarrow W^2 = \frac{1}{C^2 R_1^2}$$

$$\Rightarrow W = \frac{1}{CR_1} \Rightarrow f_u = \frac{1}{2\pi CR_1}$$

$$f_o = \frac{1}{2\pi \cdot 47 \cdot 10^9 R_2} = 4 \cdot 10^3$$

$$\Rightarrow R_2 = \frac{1}{2\pi \cdot 47 \cdot 10^9 \cdot 4 \cdot 10^3} = 8.5 \cdot 10^3 \Omega$$

2008-01-17

(5)

Problem #4

Capacitor Impedance is 200Ω . What is the Capacitance?

$$Z_C = \frac{1}{j\omega C} \quad |Z_C| = 200\Omega$$

$$\Rightarrow |\frac{1}{j\omega C}| = 200 \Rightarrow \frac{1}{\omega C} = 200 \Rightarrow C = \frac{1}{\omega 200}$$

What is ω ? Current is given as $i = 0.05 \sin(100\pi t) A \Rightarrow \omega = 100\pi$.

$$C = \frac{1}{100\pi \cdot 200} = 15.9 \mu F$$

$$U_1 = 5.0 \sin(100\pi t) V$$

$$U_2 = 10.0 \sin(100\pi t - \frac{\pi}{2}) V$$

The input Voltage:

$$\begin{aligned} V_{in} &= U_1 + U_2 \\ &= 5.0 \sin(100\pi t) + 10.0 \sin(100\pi t - \frac{\pi}{2}) \\ &= 5.0 \sin(100\pi t) - 10.0 \cos(100\pi t) \\ &= \sqrt{5.0^2 + 10.0^2} \sin(100\pi t + \tan^{-1} \frac{-10.0}{5}) \\ &\approx 11.2 \sin(100\pi t - 1.1) \end{aligned}$$