


Problem 1

2008-05-31

$$a) B = \frac{\mu_0 I}{2\pi r} = \frac{4\pi \cdot 10^{-7} \cdot 300}{2\pi \cdot 10} = 6 \cdot 10^{-6} \text{ T}$$

$$H = \frac{B}{\mu_0} = \frac{I}{2\pi r} = \frac{300}{2\pi \cdot 10} \approx 4.7746$$

b)

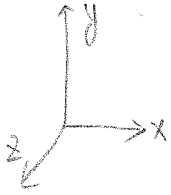

$$\vec{F}_m = q \vec{v} \times \vec{B}$$

$$\vec{v} = v \hat{x}$$

$$\vec{B} = B \hat{z}$$

$$\begin{aligned} \vec{F}_m &= q v \hat{x} \times B \hat{z} \\ &= q v B (-\hat{y}) \end{aligned}$$



For electron, q is negative, so $\vec{F}_m = |F_m| \hat{y}$

The positive charge will stay at the lower part of the antenna, and the upper part of the antenna becomes negatively charged.

c) By balance.

$$F_e = F_m \Rightarrow qE = qvB \Rightarrow E = vB$$

$$U = \int_a^b E \cdot dr$$

$$= \int_a^b \frac{v \mu_0 I}{2\pi r} dr = \frac{v \mu_0 I}{2\pi} \int_a^b \frac{1}{r} dr = \frac{v \mu_0 I}{2\pi} [\ln r]_a^b = \frac{v \mu_0 I}{2\pi} \ln\left(\frac{b}{a}\right)$$

$$\approx 3.33 \cdot 10^{-5} \cdot 0.0953$$

$$\approx 0.19 \text{ mV}$$

d) When the current I is AC. then the \vec{B} is a function of time.

$\vec{F} = q \vec{v} \times \vec{B}$ is also a function of time, which makes the electron and positive charge move up and down constantly. With the same frequency.


~~$F_m = Fe$~~

~~At the first half period, the electron will move up and down. the positive charge will~~

2008-05-31

P 244 Exempel 15.2

Problem 2 close switch at $t=0$

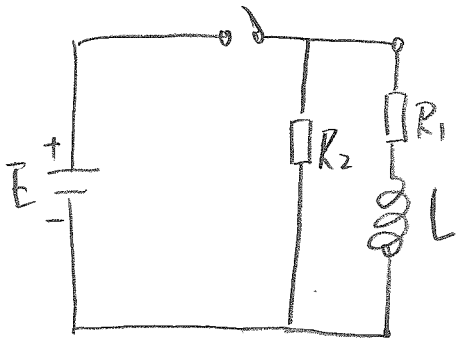

$$E = 120\text{V}$$

$$R_1 = 50\Omega$$

$$R_2 = 500\Omega$$

$$L = 100\text{mH}$$

a) write an expression for current i through L as a function of time. Specify the maximum value of current i . Calculate how long time it takes for current i through the inductor be 75% of the maximum value

b) After long time open the switch. Calculate the voltage over R_2 directly after switched off.

a) After switch on.

$$E = R_1 i + L \frac{di}{dt} \Rightarrow i = \frac{E}{R_1} (1 - e^{-t/4R_1}) \Rightarrow i = \frac{E}{R_1} (1 - e^{-t/2L})$$

$$i_{\max} = \frac{E}{R_1} = \frac{120\text{V}}{500\Omega} = 0.24\text{A}$$

$$\tau = \frac{L}{R_1} = \frac{100 \cdot 10^{-3}}{50} = 2 \cdot 10^{-3}$$


$$75\% \cdot i_{\max} = i_{\max} \cdot (1 - e^{-t/2L})$$

$$\Rightarrow e^{-t/2L} = 0.25 \Rightarrow t \approx 277\text{ms}$$

b) $U = R_2 \cdot i_{\max} = 500\Omega \cdot 0.24\text{A} = 120\text{V}$

2008-05-31

Problem 4

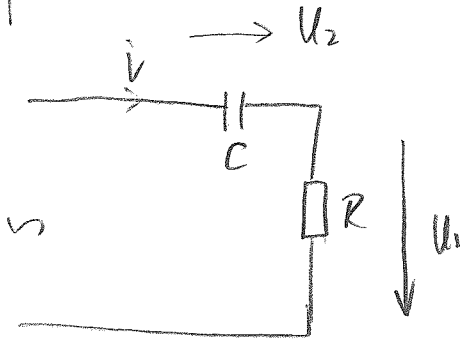

Assume

$$i = 0.050 \sin \omega t \text{ A}$$

Resistance is 100Ω . Capacitor impedance is 200Ω .

$$u_1 = R \cdot i = 5.0 \sin 100\pi t$$

$$u_2 = \frac{1}{\omega C} \hat{I} \sin(100\pi t - \frac{\pi}{2}) = 10.0 \sin(100\pi t - \frac{\pi}{2}) \text{ V}$$

Calculate the input voltage and capacitance C

$$Z_C = \frac{1}{\omega C} = 200 \Omega$$

$$\omega = 100\pi$$

$$\Rightarrow C = \frac{1}{\omega Z_C}$$

$$= \frac{1}{100\pi \cdot 200} = 15.9 \mu\text{F}$$

The input voltage:

$$u_{in} = u_R + u_C$$

$$= 5.0 \sin 100\pi t + 10.0 \sin(100\pi t - \frac{\pi}{2})$$

$$= 5.0 \sin 100\pi t - 10.0 \cos 100\pi t$$

$$= \sqrt{5.0^2 + 10.0^2} \sin(100\pi t + \arctan \frac{-10.0}{5.0})$$

$$\approx 11.2 \sin(100\pi t - 1.1) \text{ V}$$

