

Problem 1

a) According to Gauss law

$$\oint \vec{E} \cdot d\vec{s} = \frac{Q}{\epsilon}$$

Cylindrical symmetry.

$$E_r \cdot 2\pi r L = \frac{Q}{\epsilon}$$

E field inside the region between the two conductors

$$E_r \cdot 2\pi r L = \frac{\rho \cdot L}{\epsilon} \Rightarrow E_r = \frac{\rho}{2\pi \epsilon r}$$

E field outside the coaxial cable

$$E_r \cdot 2\pi r L = \frac{\rho \cdot L + (-\rho) \cdot L}{\epsilon_0} = 0 \Rightarrow E_r = 0$$

b)

$$U = \int_a^b E \cdot dr = \int_a^b \frac{\rho}{2\pi \epsilon r} \cdot dr = \frac{\rho}{2\pi \epsilon} \ln \frac{b}{a}$$

$$C' = \frac{\rho}{U} = \frac{2\pi \epsilon}{\ln b/a}$$

Problem 2

a) Ampere's current law

$$\oint_C \vec{B} \cdot d\vec{l} = \mu_0 I_r N_1 I$$

Cylindrical symmetry:

$$B_e \cdot 2\pi r = \mu_0 I_r N_1 I$$

$$B_e = \frac{\mu_0 I_r N_1 I}{2\pi r}$$

$$b) \Phi_B = \int_S \vec{B} \cdot d\vec{s} = \int_a^b \int_0^h B_e \cdot dz dr$$

$$= h \int_a^b B_e dr$$

$$= \frac{\mu_0 I_r N_1 I \cdot h}{2\pi} \ln \frac{b}{a}$$

$$e = - N_2 \frac{d\Phi_B}{dt} = - \frac{\mu_0 I_r N_1 N_2 \cdot h}{2\pi} \ln \frac{b}{a} \frac{dI}{dt}$$

$$= - \frac{4\pi \cdot 10^{-7} \cdot 2500 \cdot 2000 \cdot 500 \cdot 2 \cdot 10^{-2}}{2\pi} \ln \frac{15}{10} \cdot 200 \pi \cdot$$

$\cdot 2 \text{ GS}(200\pi t)$

$$= 5.095 \cdot 10^3 \text{ GS}(200\pi t) \text{ V}$$

$$= 5.095 \text{ GS}(200\pi t) \text{ kV}$$

Problem 3

$$a) I_C = 0; \quad I_L = I_R = \frac{U}{R} = \frac{10 \text{ V}}{50 \Omega} = 0.2 \text{ A}$$

$$b) \bar{U} = 10 e^{j1000t}$$

$$\bar{Z} = R + \frac{1}{j\omega C + \frac{1}{j\omega L}}$$

$$= R + \frac{1}{\frac{1 - \omega^2 LC}{j\omega L}}$$

$$= R + \frac{j\omega L}{1 - \omega^2 LC}$$

$$= \frac{R(1 - \omega^2 LC) + j\omega L}{1 - \omega^2 LC}$$

$$\bar{I}_R = \frac{\bar{U}}{\bar{Z}} = \frac{\bar{U}(1 - \omega^2 LC)}{R(1 - \omega^2 LC) + j\omega L} = (0.017 - j0.055) e^{j1000t}$$

$$\bar{I}_C = \bar{I}_R \cdot \frac{\bar{Z}_L}{\bar{Z}_C + \bar{Z}_L} = \bar{I}_R \cdot \frac{-\omega^2 LC}{1 - \omega^2 LC} = (-0.011 + j0.037) e^{j1000t}$$

$$\bar{I}_L = \bar{I}_R \cdot \frac{\bar{Z}_C}{\bar{Z}_C + \bar{Z}_L} = \bar{I}_R \cdot \frac{1}{1 - \omega^2 LC} = (0.028 - j0.092) e^{j1000t}$$

Problem 4

$$\bar{I} \left(R_1 + \frac{1}{j\omega C_1} \right) = \bar{U}_{in} \Rightarrow \bar{I} = \frac{\bar{U}_{in}}{R_1 + \frac{1}{j\omega C_1}}$$

$$\bar{I} \left(\frac{1}{R_2 + j\omega C_2} \right) + \bar{U}_{out} = 0$$

$$\Rightarrow \bar{U}_{out} = -\bar{I} \cdot \frac{1}{R_2 + j\omega C_2}$$

$$= -\frac{\bar{U}_{in}}{R_1 + \frac{1}{j\omega C_1}} \cdot \frac{1}{R_2 + j\omega C_2}$$

$$\Rightarrow \frac{\bar{U}_{out}}{\bar{U}_{in}} = -\frac{j\omega C_1}{1 + j\omega R_1 C_1} \cdot \frac{R_2}{1 + j\omega R_2 C_2}$$

Problem 5

THE UNIVERSITY OF

a)

Image 1 \leftrightarrow D

Image 2 \leftrightarrow E

Image 3 \leftrightarrow C

Image 4 \leftrightarrow B

Image 5 \leftrightarrow A

b) ramp filter, which is sort of high-pass filter.

The reason is to make the reconstruction less blurred,

and to enhance the fine structures in the image.