

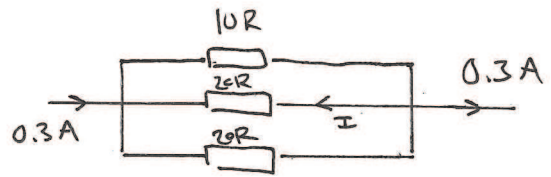


7

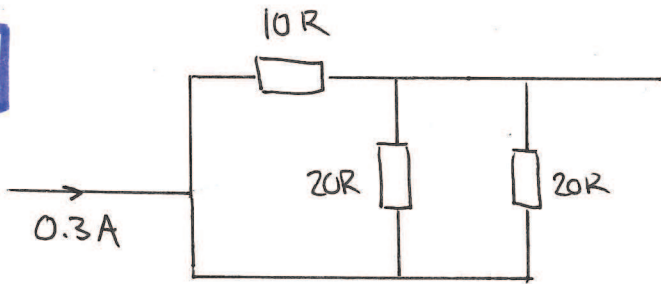
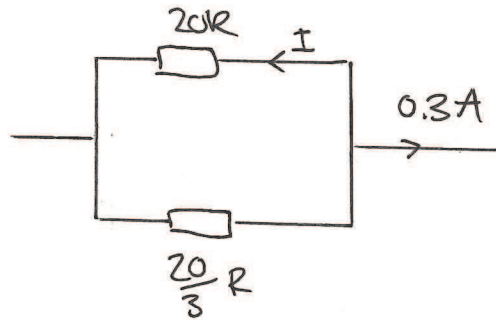
$$\frac{10R \cdot 20R}{10R + 20R} = \frac{20}{3}R$$




strömdelning

$$I_a = -I = 0.3 \frac{\frac{20}{3}R}{\frac{20}{3}R + 20R} = 0.075 \text{ A}$$

$$I = -0.075 \text{ A}$$



10

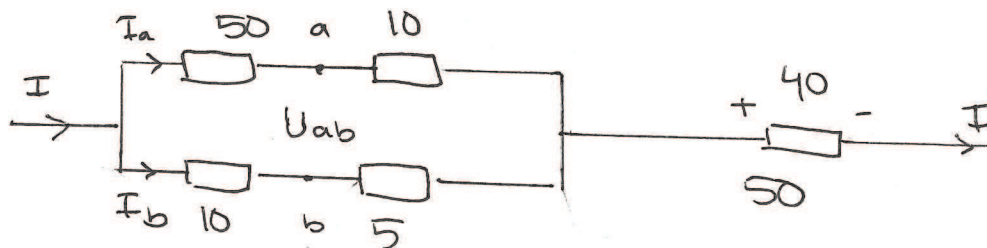

1. Bestäm  $I = \frac{40}{50} = 0.8 \text{ A}$

2. strömdelning

$$I_a = I \cdot \frac{10+5}{(10+5)+(50+10)} = 0.16 \text{ A}$$

$$I_b = I - I_a = 0.8 - 0.16 = 0.64 \text{ A}$$


3. Spänningsfall över  $50 \Omega$  resp  $10 \Omega$

$$U_1 = 50 \cdot 0.16 = 8V$$



$$U_2 = 10 \cdot 0.64 = 6.4V$$

$$\left. \begin{array}{l} U_1 = 8V \\ U_2 = 6.4V \end{array} \right\} U_{ab} = 8 - 6.4 = 1.6V$$

15 SPP

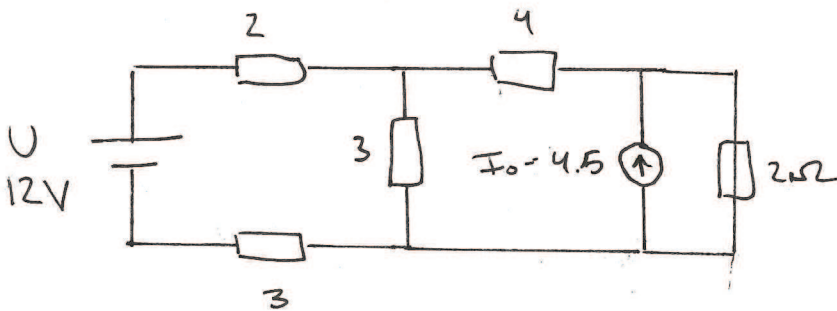


(1) Kortslut  $U$ , bryt  $I_0$  (2)

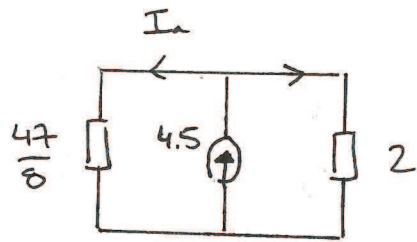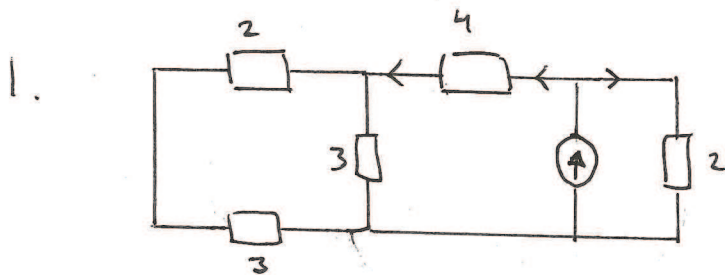


$$I_a = \frac{2}{2 + \frac{47}{8}} I_0 = 1.143 A$$

Nästa strömdeln:  $I'' = I_a \frac{3}{3+3+2} = 1.143 \cdot \frac{3}{8} = 0.429 A$

2. Bryt  $I_0$

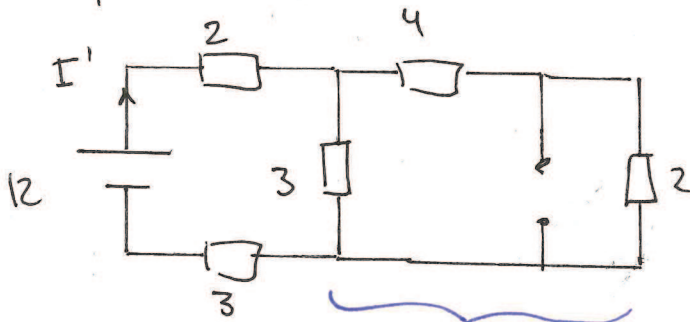


$$\frac{6 \cdot 3}{3+6} = 2 \Omega$$

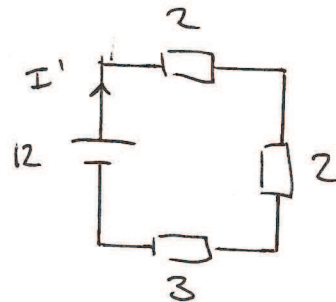

$$I' = \frac{12}{7} A$$

Svar:  $I = I' - I'' = \frac{12}{7} - 0.429 = 1.29 A$

[1]

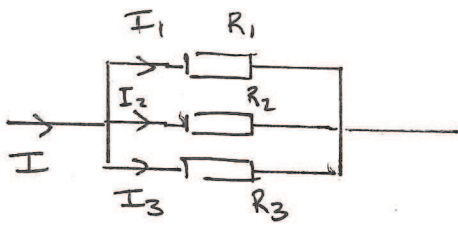

(a) K1:  $I = I_1 + I_2 + I_3$  (1)

K2:  $R_2 I_2 - R_1 I_1 = 0$  (2)


$R_3 I_3 - R_2 I_2 = 0$  (3)

$$I = I_2 \left( \frac{R_2}{R_1} + 1 + \frac{R_2}{R_3} \right) = \frac{R_2 R_3 + R_1 R_3 + R_1 R_2}{R_1 R_3} I_2$$

$$I_1 = \frac{R_2}{R_1} I_2$$

$$I_3 = \frac{R_2}{R_3} I_2$$

(b)

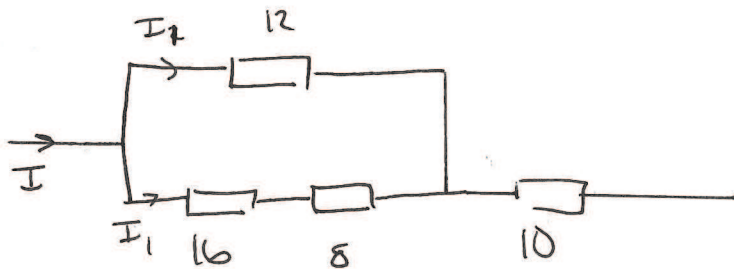



$$I_2 = 4 \text{ A}$$

$$I = I_1 + I_2$$

$$V = (16 + 8) I_2 = 96 \text{ V}$$


$$V = 12 \cdot I_1 = 96 \text{ V} \implies I_1 = \frac{96}{12} = 8 \text{ A}$$

$$I = 8 + 4 = 12 \text{ A}$$

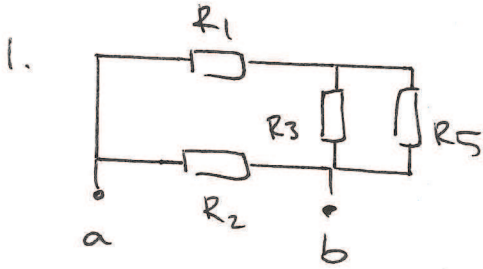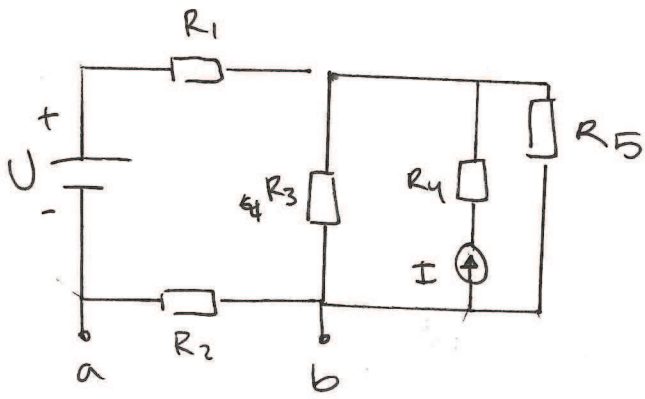

.....

4

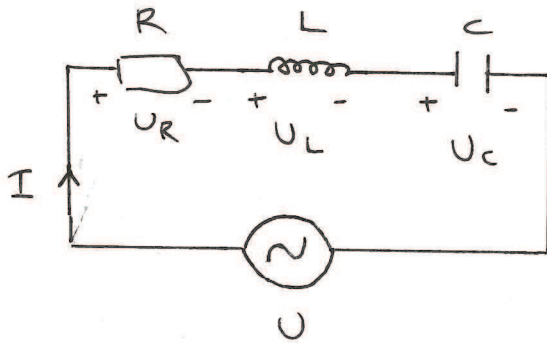

Resonans:  $U_L = U_C$


$$\cancel{\omega L I} = \frac{1}{\cancel{\omega C}} I$$

$$\underline{\omega L = \frac{1}{\omega C}}$$

$$\underline{U = U_R = R I}$$

(c) vid resonans:  $I = I_{\max}$

$$\bar{Z} = \bar{Z}_{\min} = R$$

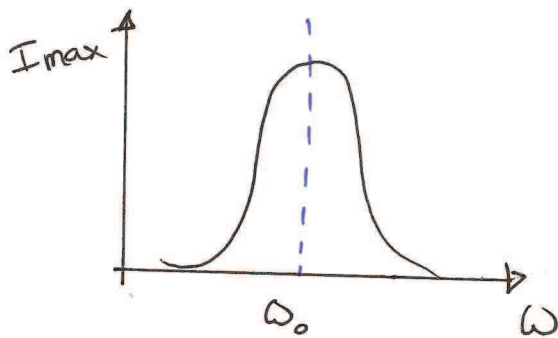

$$\omega_0 < \omega$$


$\omega L$  minskar

$\frac{1}{\omega C}$  ökar


30

(1)

$U$   
220V  
50Hz

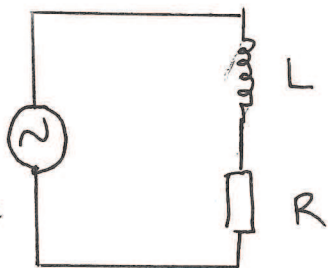

$$S = \sqrt{P^2 + Q^2}$$

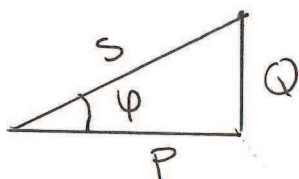

$$P = 4 \text{ kW}$$

$$Q = 3 \text{ kVAR}$$

$$S = U \cdot I = \sqrt{P^2 + Q^2}$$

$$I = \frac{\sqrt{P^2 + Q^2}}{220} = 22.7 \text{ A}$$


$$P = RI^2 \rightarrow R = \frac{P}{I^2} = \frac{4000}{515} = 7.8 \Omega$$

{ Obs! Håll koll på skillnaden:  $u(t)$ ,  $U$ ,  $\hat{U}$ ,  $\bar{U}$  }

(2) Parallell C kopplas in      Sökt:  $C$

vilket:  $\cos \varphi = 1$

220V  
50Hz

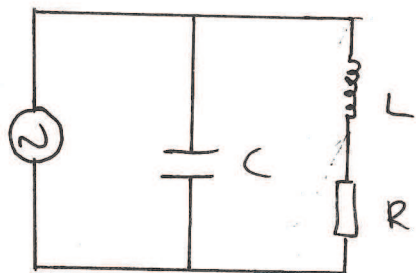

utan C:

$$I = 22.7 \text{ A}, R = 7.8 \Omega, U = 220 \text{ V}$$

$$\omega = 100 \pi$$

$$\bar{Z} = R + j\omega L$$

$$\bar{Z} = \frac{\bar{U}}{\bar{I}} \quad I = \frac{U}{|\bar{Z}|} = \frac{220}{\sqrt{R^2 + (\omega L)^2}} = 22.7 \text{ A}$$



$$\cancel{22.7} =$$

$$220 = 22.7 \sqrt{(7.8)^2 + (\omega L)^2}$$

$$(\omega L)^2 = \frac{48400 - 31350}{515.3} = 33.1$$

$$L = \frac{\sqrt{33.1}}{100\pi} = 0.018 \text{ H}$$

$$\bar{Z} = R + j\omega L = 7.8 + j \cdot 100\pi \cdot 0.018 = \cancel{7.8 + 5.16j} \quad 7.8 + 5.65j$$

$$\cancel{\arctan \frac{5.65}{7.8}} \quad \arctan \frac{5.65}{7.8} = 35.9^\circ \approx 36^\circ$$

$$\arctan \frac{5.65}{7.8} = 35.9^\circ \approx 36^\circ$$

$$I_c = I_L \sin \phi = 22.7 \sin 36 = 13.3 \text{ A}$$

$$U = I_c \frac{1}{\omega C} \rightarrow C = \frac{I_c}{\omega U}$$

$$C = \frac{13.3}{100\pi \cdot 220} = 193 \mu\text{F}$$

3

